

Printing Page(s) : 1

Paper Code :DCS-109

Roll No.

--	--	--	--	--	--	--	--	--	--

BCA-7
1st Year Examination, Calendar Batch 2017
Computer Organization

Time : 3 Hours]

[Max. Marks : 100

*Note. Attempt any **Five** questions. All questions carry equal marks.*

- Q.1** Explain the role of fetch, decode and execution in instruction cycle. Draw the flow chart?
- Q.2** Explain in detail all the types of Adders and Subtractors? How a full adder is built using half adder.
- Q.3** What is the basic advantage of priority interrupt over a non priority interrupt?
- Q.4** Explain how S- R flip-flop is realized by NOR Gate and by NAND gate.
- Q.5** Explain the functional diagram of 16- bit Micro processor (8086).
- Q.6** Explain all type of counters with their block diagram.
- Q.7** Explain instruction format. What are the various types of instruction format? Discuss them with suitable example?
- Q.8** What are Logic gates? Explain in detail all type of logic Gates and design AND, OR, NOT gates using universal gates.